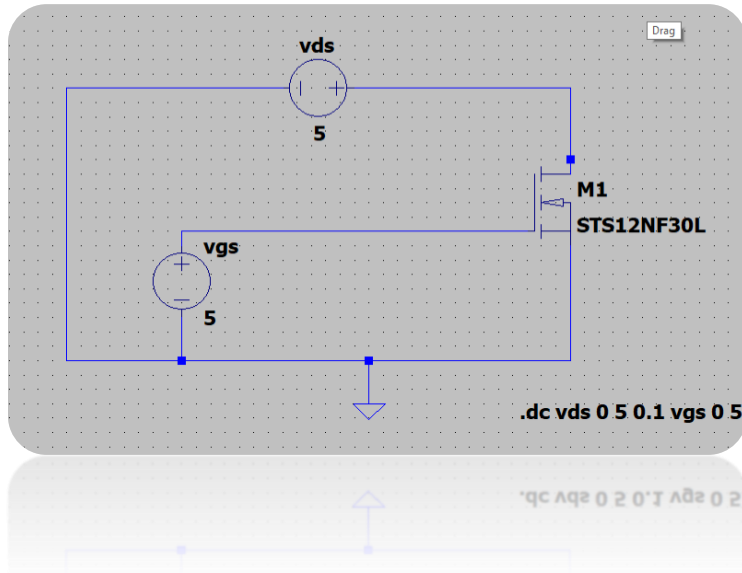
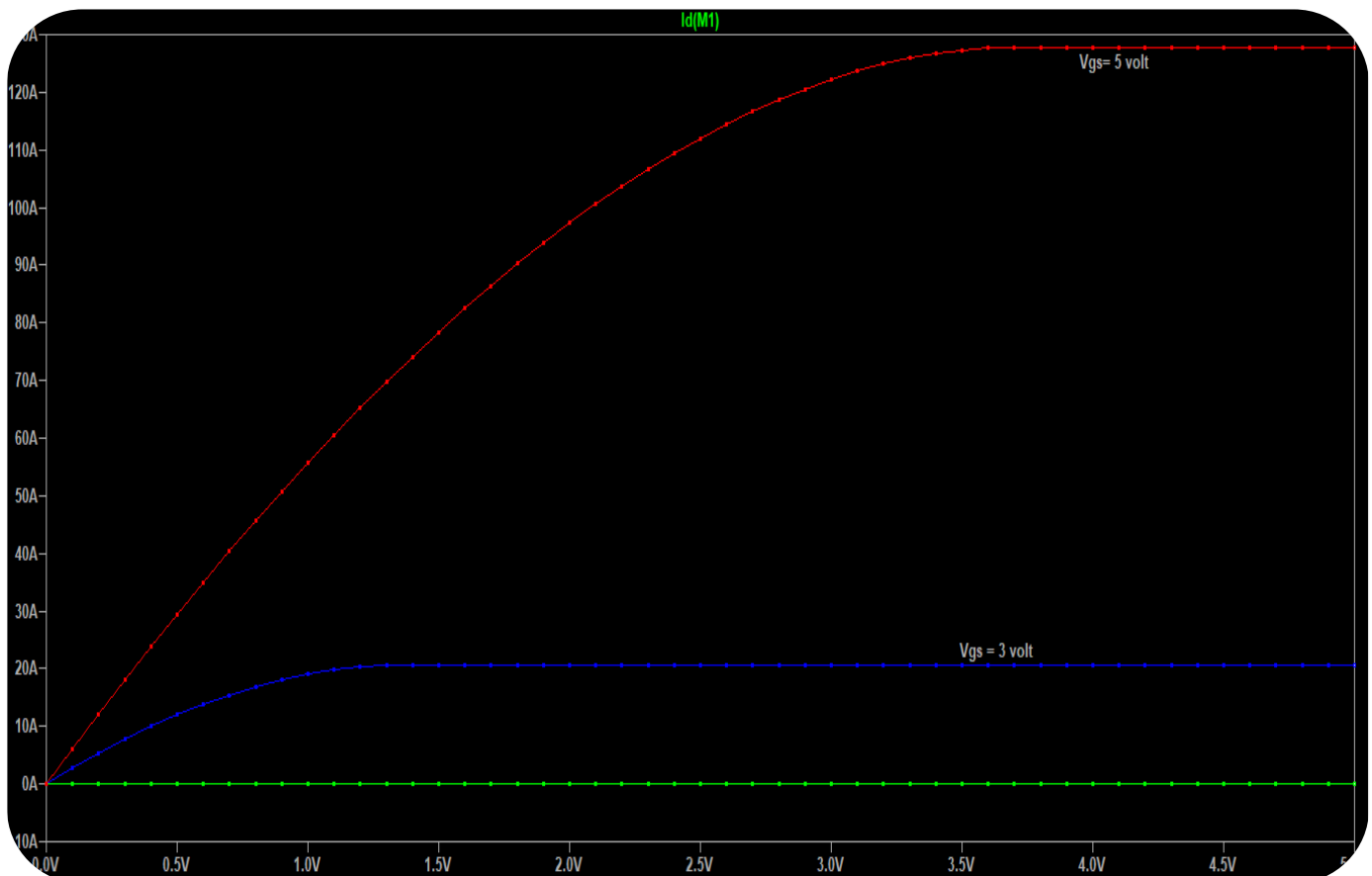


Homework #3: NMOS transistor analysis Assignment



The circuit we have to simulate it

The output simulation Diagram



To find β and V_T , I took two points from the previous curve in the saturation region and I substituted the points in the saturation equation as following

The two points is

Point 1

$V_{ds} = 4.9$ volt

$I_{ds} = 20.6$ Ampere

$V_{gs} = 3$ volt

Point 2

$V_{ds} = 4.9$ volt

$I_{ds} = 127.74$ Ampere

$V_{gs} = 5$ volt.

$$I_{ds} = \frac{\beta}{2} (V_{gs} - V_T)^2 \quad \text{The Sat Equation.}$$

$$4.9 = \frac{\beta}{2} (3 - V_T)^2 \quad \longrightarrow \quad \frac{6.4}{\sqrt{\beta}} + V_T = 3$$

$$127.74 = \frac{\beta}{2} (5 - V_T)^2 \quad \longrightarrow \quad \frac{15.9837}{\sqrt{\beta}} + V_T = 5$$

By solving the previous two Equations

$$\beta = 22.864$$

$$V_T = 1.657 \text{ volt.}$$